

Lab-Report 6

Course Code: CSE-404

Course Name: VLSI Design Lab

Submitted By

Name: Md. Jahirul Islam

ID: 181-017-042

Department of CSE

Submitted To

Shaiyek Md. BulandTaslim

Lecturer

Department of EEE

Submitted Date: 15-08-2021


Experiment Name:A 2-input NAND gate is diving a 2-input NOR gate and an inverter using MICROWIND.

Objective:A 2-input NAND gate is diving a 2-input NOR gate and an inverter and see the performance and output wave shape.


TruthTable:

A	B	C	NAND (AB)	NOR	INVERTER
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	0	0
1	1	0	0	1	1
1	1	1	0	0	1


Microwind Design:

 

Microwind Output:

 




DSCH2 Input:


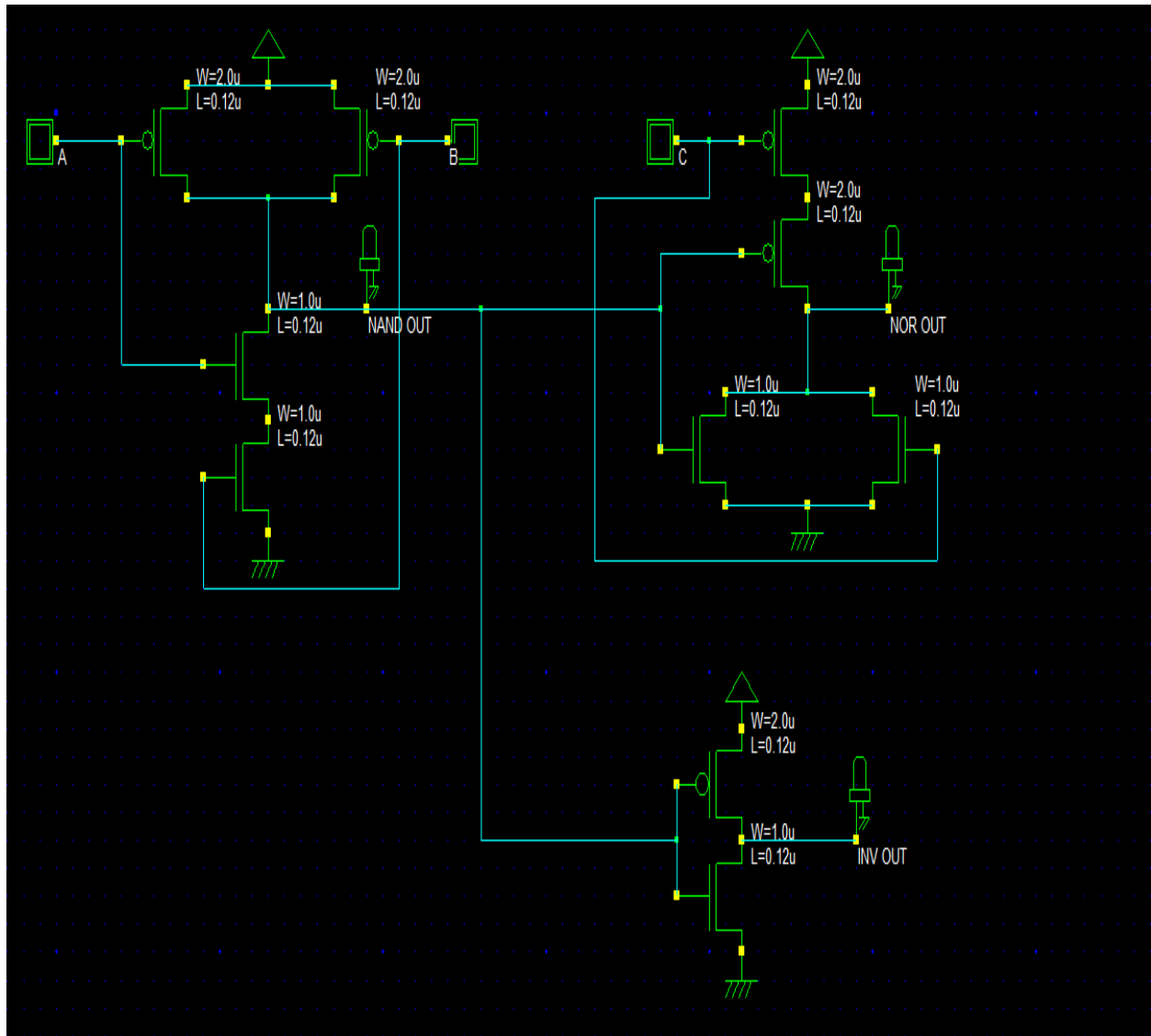


DSCH2 Output:

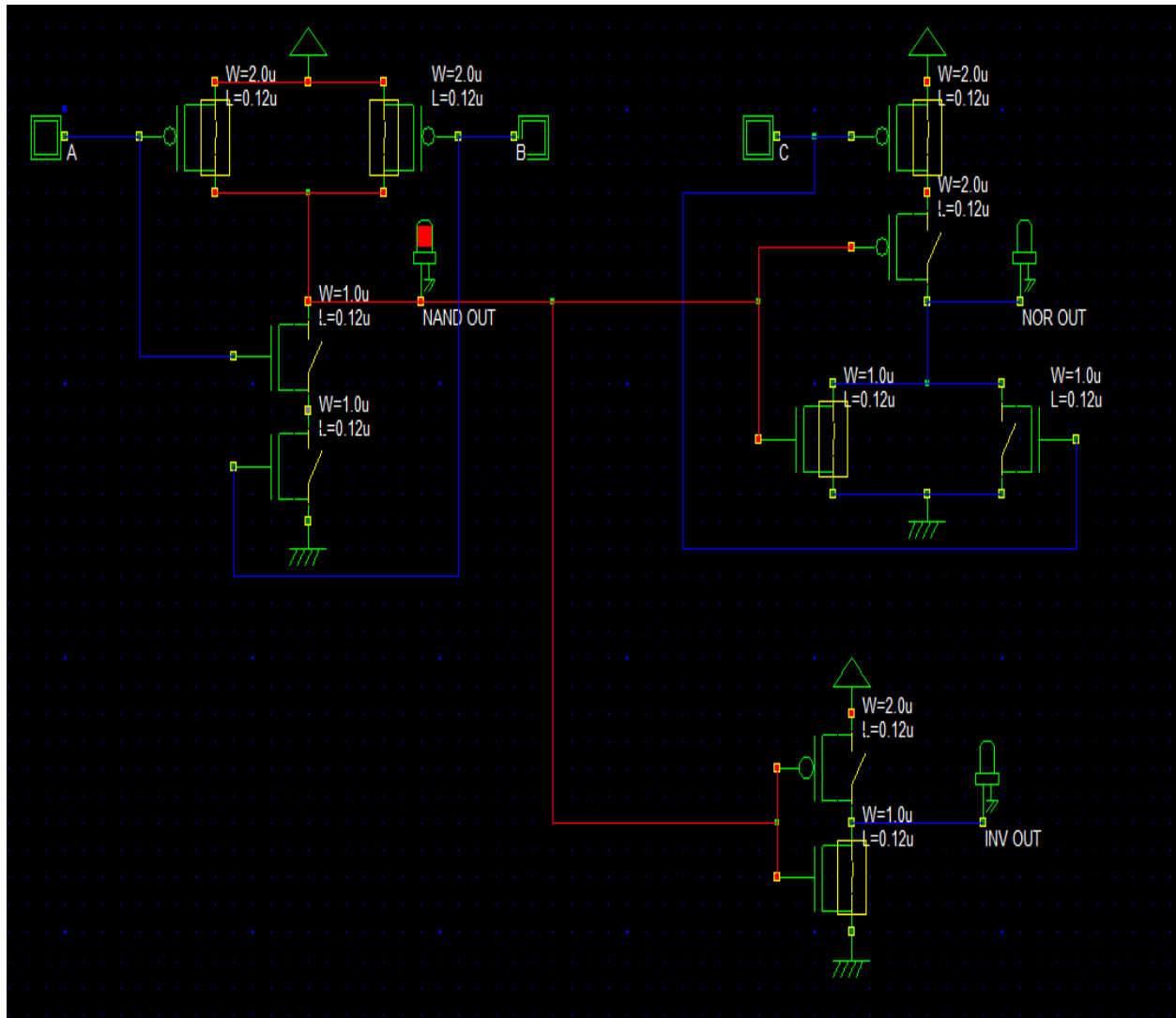All the outputs are same as the truth table. Here I have given some sample output.



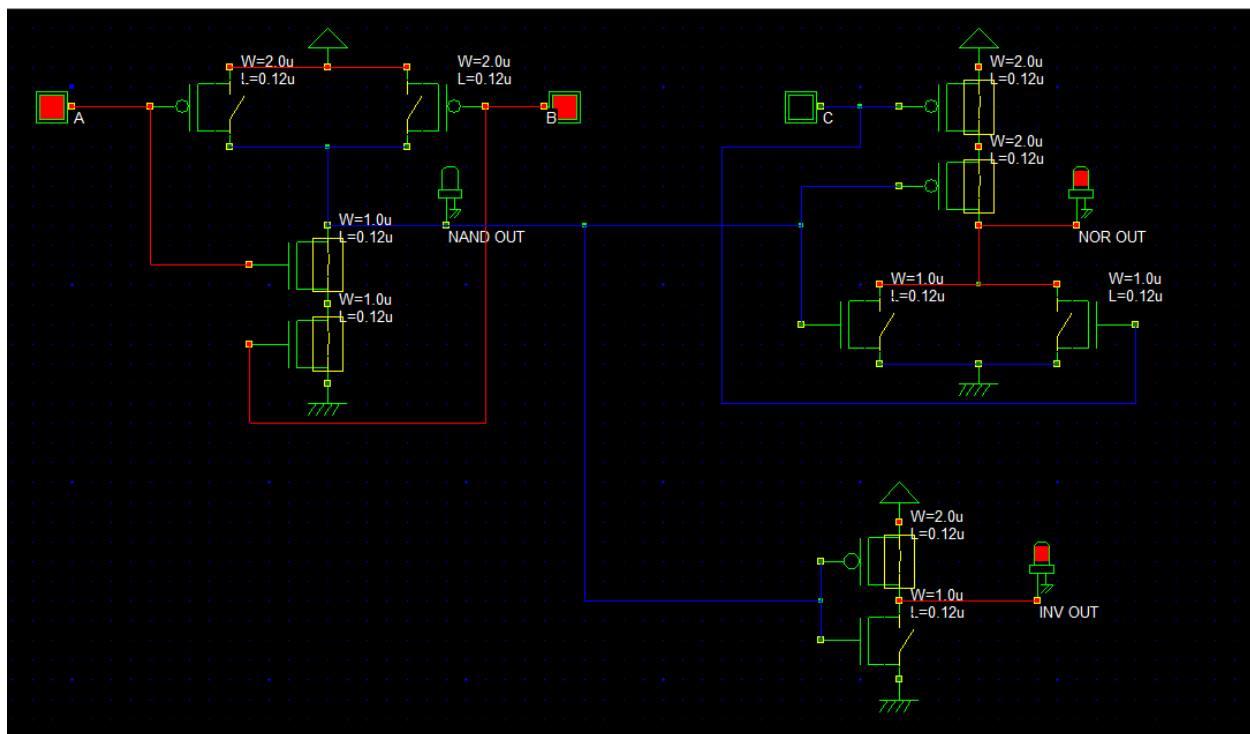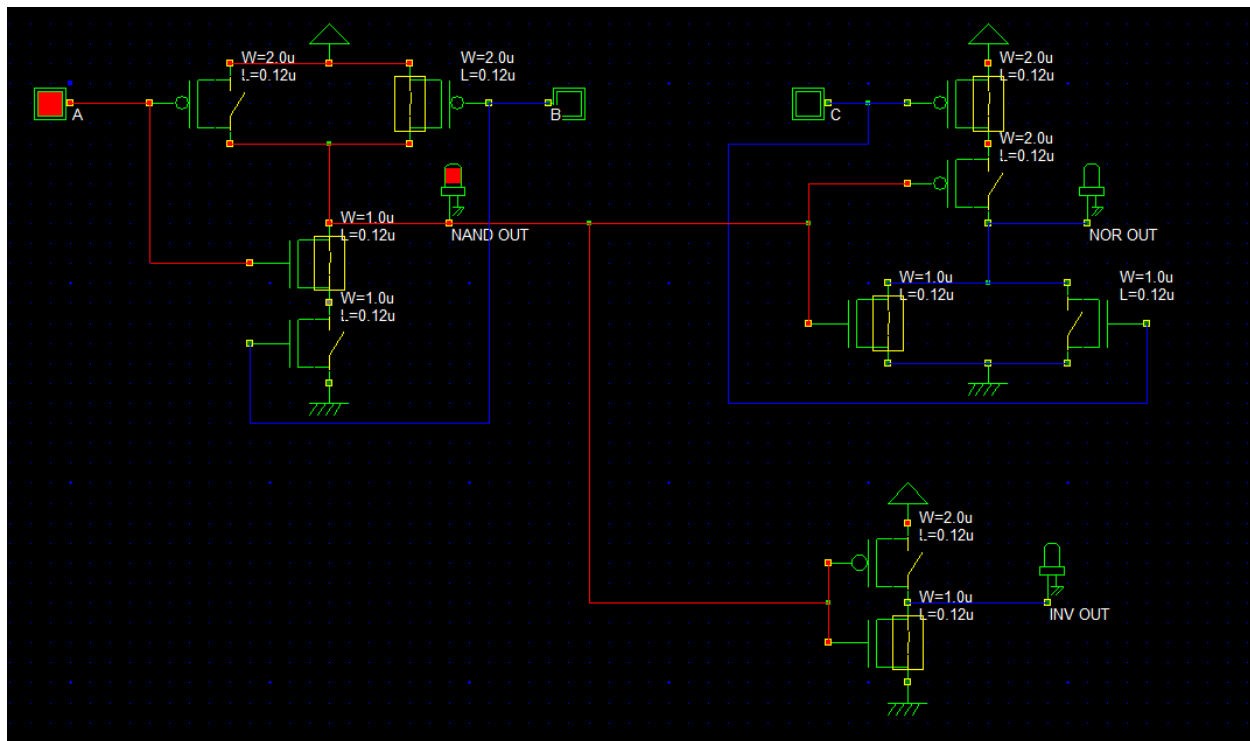

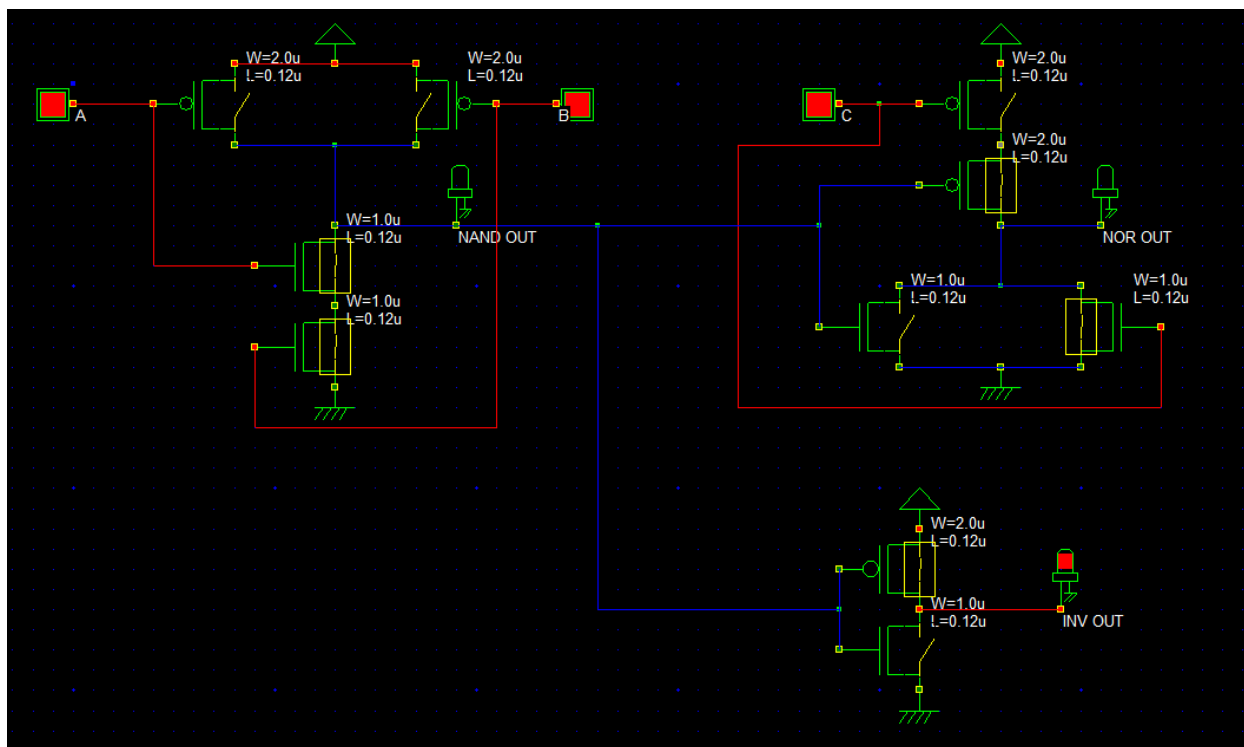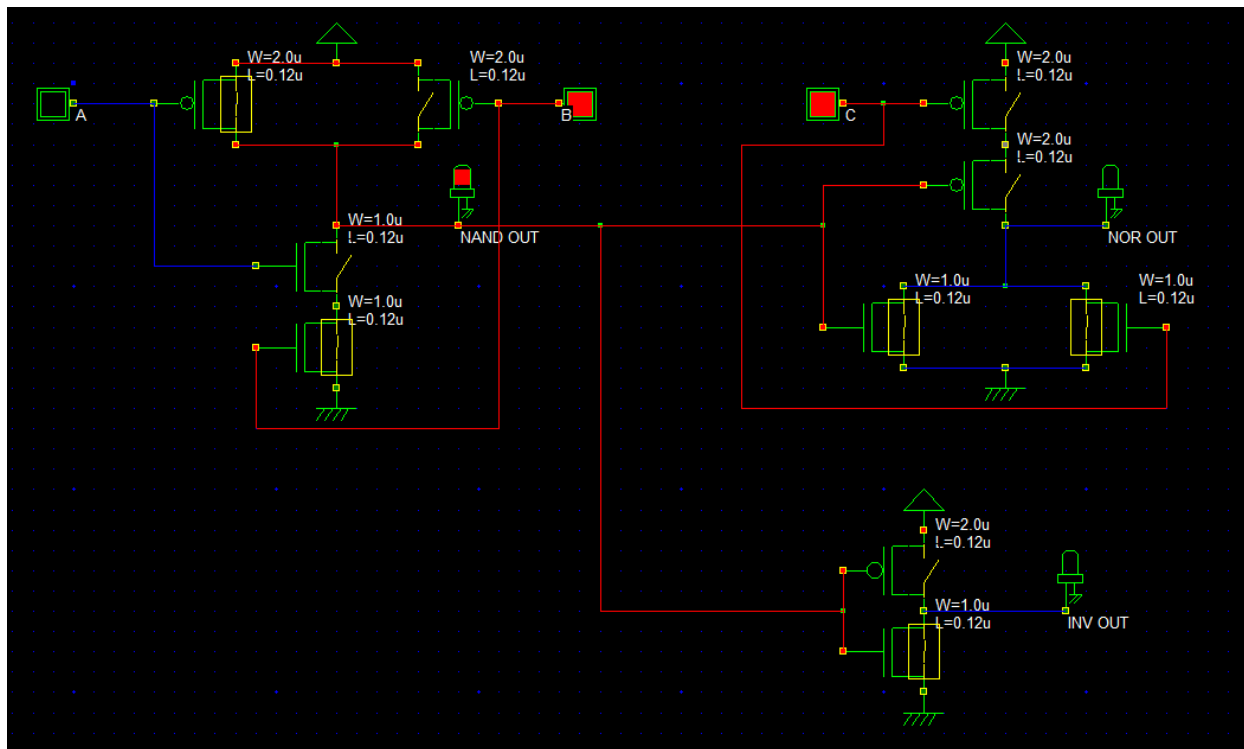

Code:

Verilog, Hierarchy and Netlist

Verilog | Hierarchy | Netlist | Critical path

```
// DSCH 2.7f
// 15/08/2021 1:04:20
// example

module example( C,A,B,INVOUT,NANDOUT,NOROUT);
  input C,A,B;
  output INVOUT,NANDOUT,NOROUT;
  pmos #(52) pmos(NANDOUT,vdd,A); // 2.0u 0.12u
  pmos #(52) pmos(NANDOUT,vdd,B); // 2.0u 0.12u
  nmos #(52) nmos(NANDOUT,w4,A); // 1.0u 0.12u
  nmos #(10) nmos(w4,vss,B); // 1.0u 0.12u
  pmos #(10) pmos(w7,vdd,C); // 2.0u 0.12u
  pmos #(24) pmos(NOROUT,w7,NANDOUT); // 2.0u 0.12u
  nmos #(24) nmos(NOROUT,vss,NANDOUT); // 1.0u 0.12u
  nmos #(24) nmos(NOROUT,vss,C); // 1.0u 0.12u
  pmos #(17) pmos(INVOUT,vdd,NANDOUT); // 2.0u 0.12u
  nmos #(17) nmos(INVOUT,vss,NANDOUT); // 1.0u 0.12u
endmodule

// Simulation parameters in Verilog Format
always
#1000 C=~C;
#2000 A=~A;
#4000 B=~B;


// Simulation parameters
// C CLK 10 10
// A CLK 20 20
```

Information


Module name (8 char. max)

☒ Add gate delay info
☒ Append simulation informations
☐ Add labels as comments

The Verilog file has 29 lines
The design includes 22 symbols
The circuit has 9 nodes

 OK

Compiled Verilog on Microwind:

 

Output:

